 


Youssef Abdelmaksoud

Implement n-bits full ALU

Description: The ALU performs simple addition, subtraction, multiplication, division, and logic operations, such as OR and AND. The memory stores the program's instructions and data.

Name of Main Module: ALU



Options of OpCode:

OpCode	Operation
0000	Op1 AND Op2
1111	Op1 OR Op2
1001	Op1 + Op2
0110	Op1 – Op2

Notes on variables of the ALU:

- **N**: the size of the input/output of the ALU. It should be variable set to 32 in the ALU module.
- **OpCode**: chooses which operation to apply on the operands
- **Op1**: first input, n-bit in length
- **Op2**: second input, n-bit in length
- **Cin**: Carry input (to be considered in addition/subtraction operations) • **Cout**: Carry output (to be considered in addition/subtraction operations) • **Overflow flag**: if in addition, oFlag is turned on when:
 - The sum of two numbers with the sign bit off yields a result number with the sign bit on. ✦ $0100 + 0100 = 1000 \Rightarrow$ overflow flag is turned on.
 - The sum of two numbers with the sign bit on yields a result number with the sign bit off.
 - ✦ $1000 + 1000 = 0000 \Rightarrow$ overflow flag is turned on.
 - Mixed-sign addition never turns on the overflow flag.
 - For more details to understand it, check the link [here](#).
 - If in subtraction, same rules apply between Op1 and 2's compliment of Op2.
- **Zero Flag**: set to 1 in case the output is zero
- **Result**: output of the ALU, n-bit in length

Grading Schema:

Code Structure	4 points
Wave Window	1 point
RTL Design	1 point
Test case 1	0.5
Test case 2	0.5
Test case 3	0.5
Test case 4	0.5
Test case 5	1
Test case 6	1
(Total)	10

Testing Bench (Main):

```
module main();
  reg [31:0] op1;
  reg [31:0] op2;

  reg [3:0] opCode;
  reg Cin

  wire [31:0] result;
  wire cflag, zflag, oflag;

  ALU my_alu(OpCode, op1, op2, cin, result, cflag, zflag, oflag);

  initial
  begin
    $display("Hello, World");
    $finish ;
  end
endmodule
```

Test Cases:

1.

Type	Var. Name	Value
Input	Op1	0011001100110011001100110011
Input	Op2	1100110011001100110011001100
Input	OpCode	1111
Input	Cin	1
Output	Result	1111111111111111111111111111
Output	cFlag	0
Output	zFlag	0
Output	oFlag	0

2.

Type	Var. Name	Value
Input	Op1	0011001100110011001100110011
Input	Op2	1100110011001100110011001100
Input	OpCode	0000
Input	Cin	0
Output	Result	0000000000000000000000000000
Output	cFlag	0
Output	zFlag	1
Output	oFlag	0

3.

Type	Var. Name	Value
Input	Op1	00000000000000001111111111111111
Input	Op2	00000000000000000000000000000001
Input	OpCode	1001
Input	Cin	1
Output	Result	00000000000000001000000000000001
Output	cFlag	0
Output	zFlag	0
Output	oFlag	0

4.

Type	Var. Name	Value
Input	Op1	00000000000000000000000000001000
Input	Op2	00000000000000000000000000000001
Input	OpCode	0110
Input	Cin	0
Output	Result	0000000000000000000000000000111
Output	cFlag	0
Output	zFlag	0
Output	oFlag	0

5.

Type	Var. Name	Value
Input	Op1	11110000111100001111000011110001
Input	Op2	00001111000011110000111100001111
Input	OpCode	1001
Input	Cin	0
Output	Result	00000000000000000000000000000000
Output	cFlag	1
Output	zFlag	1
Output	oFlag	0

6.

Type	Var. Name	Value
Input	Op1	0011001100110011001100110011
Input	Op2	0100110011001100110011001100
Input	OpCode	0110
Input	Cin	1
Output	Result	1110011001100110011001100110
Output	cFlag	1
Output	zFlag	0
Output	oFlag	1